



# Serial Parallel Multiplier Design in Quantum-dot Cellular Automata

Heumpil Cho and Earl E. Swartzlander, Jr.

Application Specific Processor Group  
Department of Electrical and Computer Engineering  
The University of Texas at Austin  
Austin, TX 78712 USA



## Outline

---

- Motivation
- Quantum-dot Cellular Automata
- Serial Multiplier Designs in QCA
- Conclusions



## Motivation


# Quantum-dot Cellular Automata (QCA)

- Alternative to Transistor Technologies
  - Avoids High Power Consumption Due to Leakage Currents
- Quantum-dot Cellular Automata (QCA)
  - Emerging Nanotechnology for Electronic Circuits
    - Introduced in 1993
    - Freedom from Complicated Physics
  - High Density, Low Power Consumption, and Fast
  - Some Experimental Devices Have Been Created
- Several QCA Circuits Have Been Proposed
  - Ripple Carry Adders, Barrel Shifters, and Memories
  - Complex Designs Rare
- Key Characteristics
  - Inverters and 3-Input Majority Gates
  - Interconnect Consumes Time and Space
    - Difficult to Estimate Timing Until the Layout is Done
  - Signal Synchronization and Refresh
    - Wires Act as Latches
    - Best for Pipeline Architectures Without Feedback


 
# Basic Quantum-dot Cell



- Square Nanostructure
  - Each Cell
    - Has Four Quantum Dots
    - Can Possess a Single Electron per Dot
    - Charged With Two Electrons
  - Two Polarizations are Possible by Coulombic Repulsion




  
# Signal Propagation

- Main Roles of Cells
  - Computation, Storage, and Communication
  - Wire Dominant Design
- Series of QCA Cells
  - Act Like a Wire
  - Propagate the Signal
- Clock Zones
  - Four Clock Phases
  - Control the Signal Flow
  - Cells Are Refreshed on Every Cycle





# Fundamental Gates

- Inverter

  - Conventional Gate

- 3-Input Majority Gate


$$M(a,b,c) = a \cdot b + b \cdot c + c \cdot a$$

- 2-Input AND/OR Gate

  - Implemented by Setting One Input to a Constant

$$a \cdot b = M(a,b,0)$$



$$a + b = M(a,b,1)$$

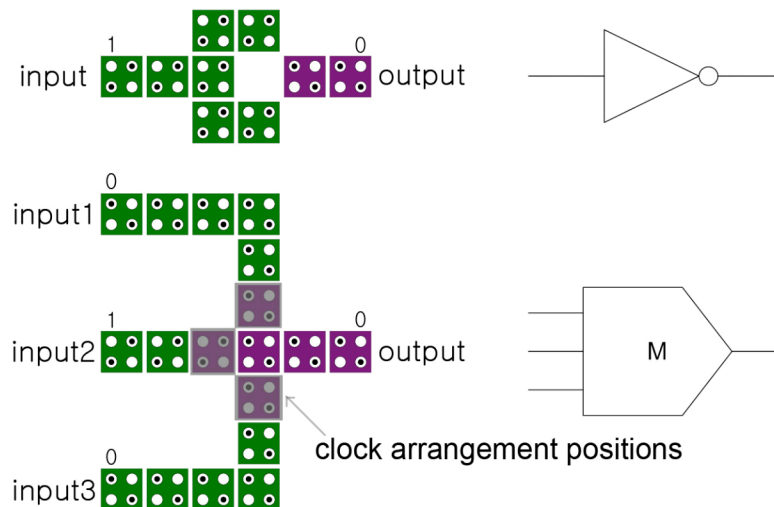


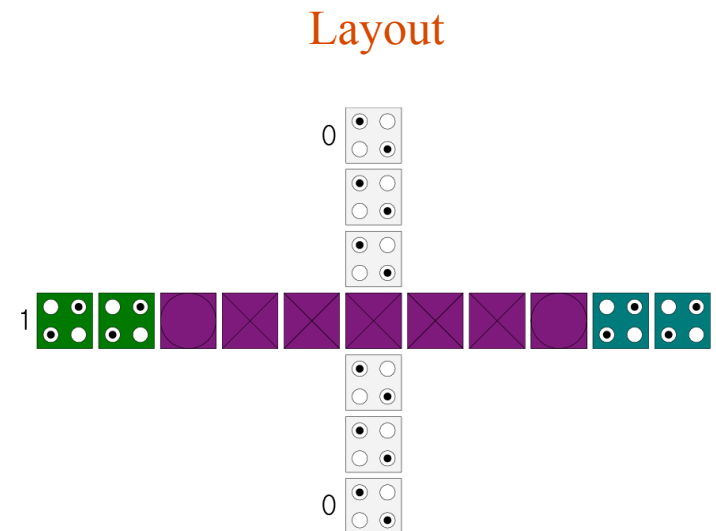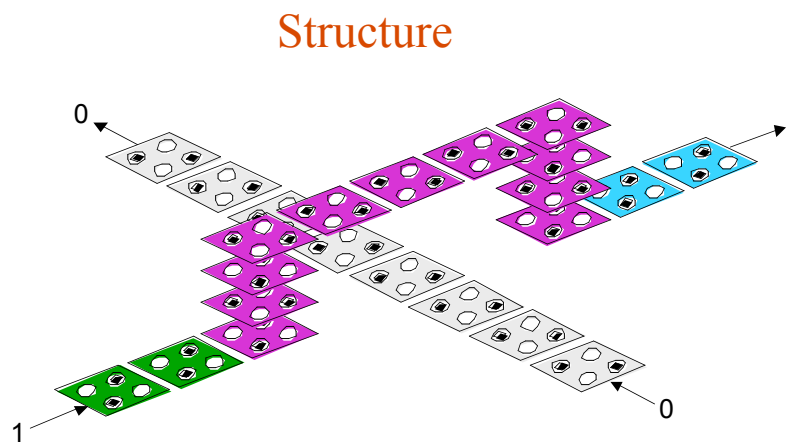
## Multi-Layer Wire Crossovers

- Use Several Layers for Crossovers
  - 3D Structure
- Pros and Cons
  - + Area Efficient Design
  - Manufacturability Issues





## QCA Circuit Design Rules

---

- Cell Size
  - Set at 20nm
    - Width and Height: 18nm
    - Quantum-dot Diameter: 5nm
    - Cell Center-to-Center Spacing: 20nm
- Size Limit on Cells Per Clock Zone
  - Limit: 15 Cells
    - Proper Propagation Delay and Reliable Signal Transmission
    - Freedom for Routing and a Reasonable Clock Zone Size
- Minimum Separation of Two Different Wires
  - The Width of Two Cells
- Clock Increment Rule
  - Increment the Clock Zone at the Clock Arrangement Positions





## Serial Parallel Multiplier Designs in QCA

---

- Multiplier Design Issues
  - A Parallel Multiplier is a Very Complex Circuit
  - Complex Circuits Often Incur Significant Delay
- Simple Structure is Desirable
  - Serial-Parallel Multiplier Design Selected
  - Filter Design Methodology is Used



# Algorithmic Design

- FIR Filter Design Example


- Delay Operator:  $Z^{-1}$

$$Z^{-1}x_i = x_{i-1}, \quad Z^{-n} = Z^{-1}Z^{-n+1}$$

- Filter Equation

$$y_i = b_0x_i + b_1x_{i-1} + b_2x_{i-2} + \dots + b_{N-2}x_{i-N+2} + b_{N-1}x_{i-N+1}$$
 
$$= \sum_{k=0}^{N-1} b_k x_{i-k} = \sum_{k=0}^{N-1} b_k Z^{-k} x_i = \left( \sum_{k=0}^{N-1} b_k Z^{-k} \right) x_i$$





## Pipelined FIR Filter Network


- Pipelined FIR Filter Output (Right-to-Left Structure)

$$= Z^{-\frac{1}{2}} \left( b_{N-1} Z^{-\frac{3}{2}(N-1)} + Z^{-\frac{1}{2}} \left( b_{N-2} Z^{-\frac{3}{2}(N-2)} + \dots + Z^{-\frac{1}{2}} (b_0 Z^0) \right) \right) x_i$$

$$= Z^{-\frac{N}{2}} b_{N-1} Z^{-(N-1)} x_i + Z^{-\frac{N}{2}} b_{N-2} Z^{-(N-2)} x_i + \dots + Z^{-\frac{N}{2}} b_0 x_i$$

$$= Z^{-\frac{N}{2}} \left( \sum_{k=0}^{N-1} b_k Z^{-k} \right) x_i$$


$$= Z^{-\frac{N}{2}} y_i$$

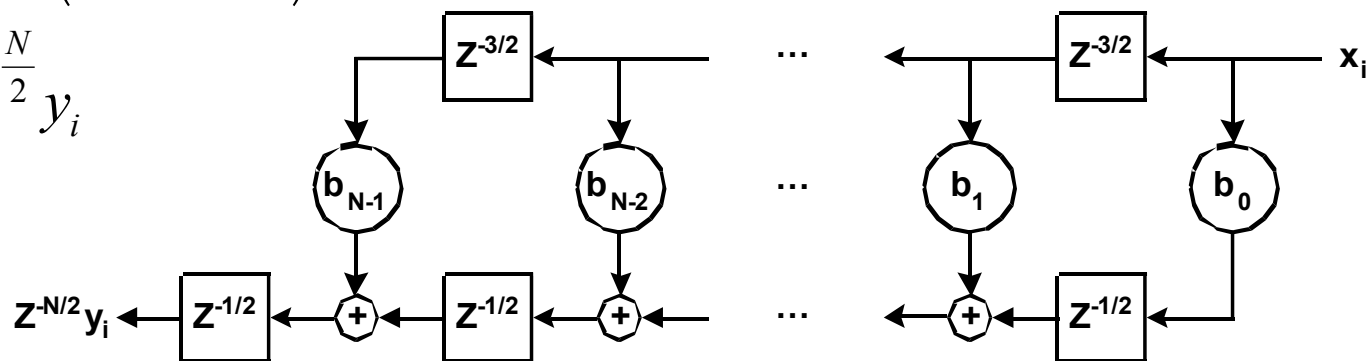



 
## Redirected FIR Filter Network

- General Structure (Right-to-Right Structure)



- Pipelined Structure

 


$$\begin{aligned}
 Z^{-\frac{1}{2}} y_i &= Z^{-\frac{1}{2}} \left( \sum_{k=0}^{N-1} b_k Z^{-k} \right) x_i \\
 &= Z^{-\frac{1}{2}} \left( \sum_{k=0}^{N-1} b_k Z^{-\frac{k}{2}} Z^{-\frac{k}{2}} \right) x_i \\
 &= Z^{-\frac{1}{2}} \left( \sum_{k=0}^{N-1} Z^{-\frac{k}{2}} b_k Z^{-\frac{k}{2}} \right) x_i
 \end{aligned}$$



 
## Multiplication Signal Flows

- Unsigned Number Multiplication
  - Bit Product Matrix and Signal Flow of Right-to-Left Structure



 
- Bit Product Matrix and Signal Flow of Right-to-Right Structure





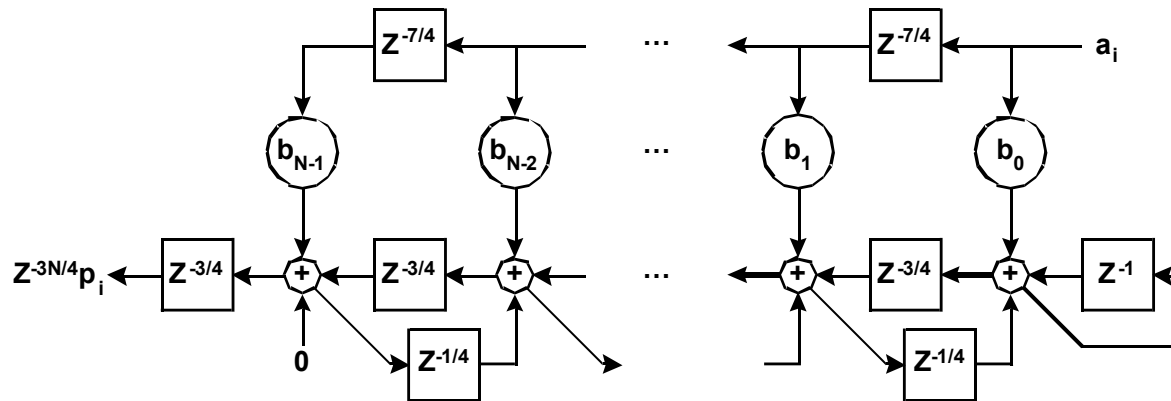
## Network Diagrams-I

- Right-to-Left Carry Shift Multiplication (CSM)



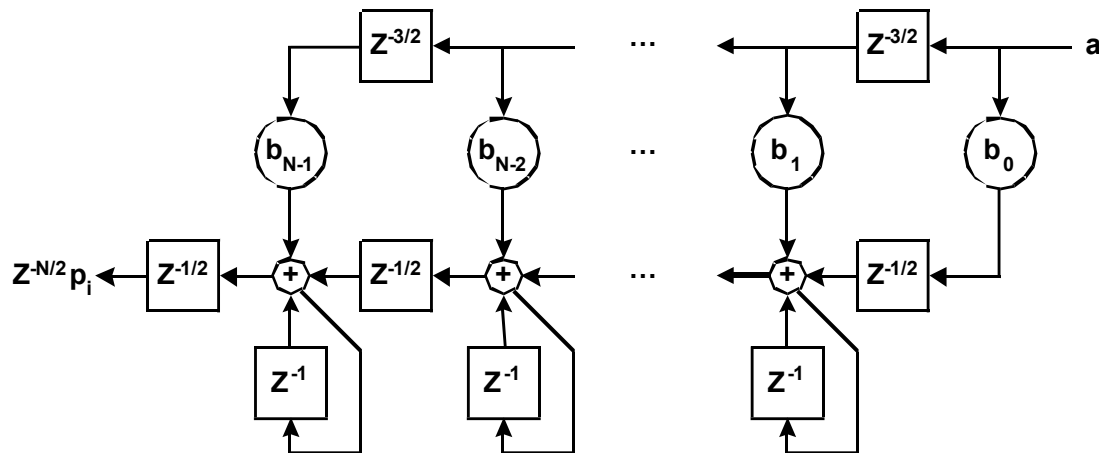
- Right-to-Left Carry Delay Multiplication (CDM)





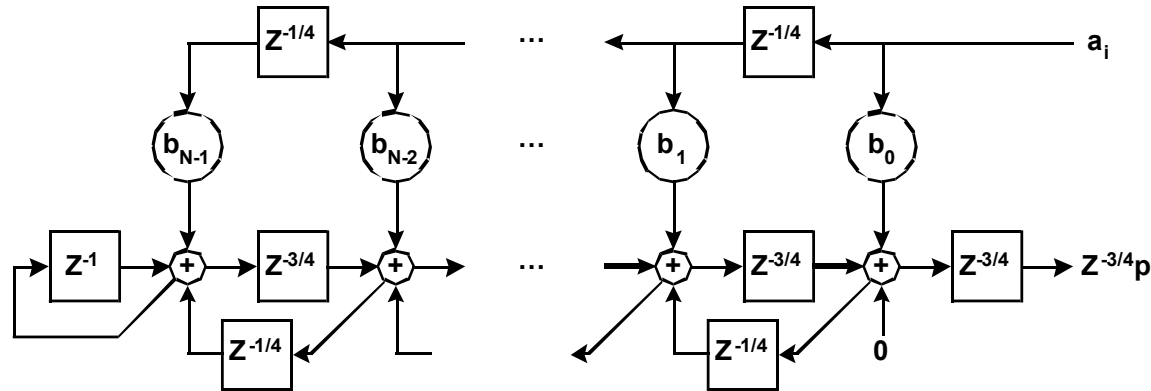
# Network Diagrams-II

- Right-to-Right Carry Shift Multiplication (CSM)



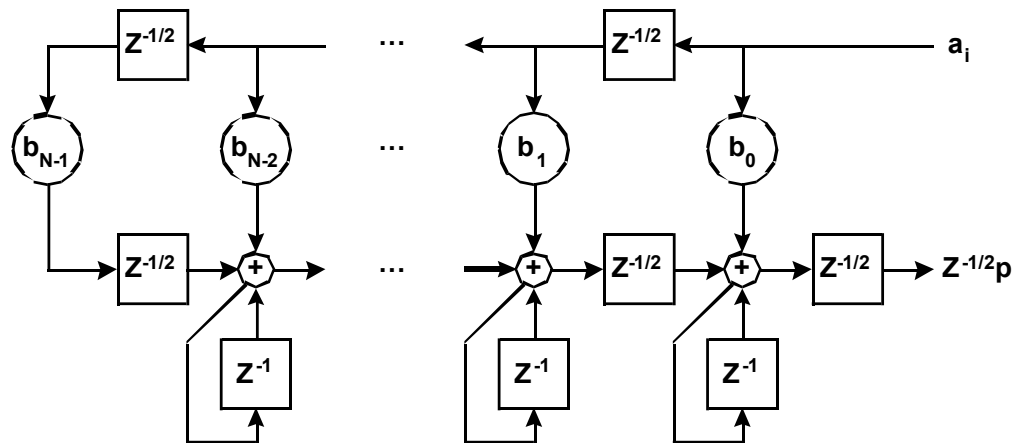
- Right-to-Right Carry Delay Multiplication (CDM)




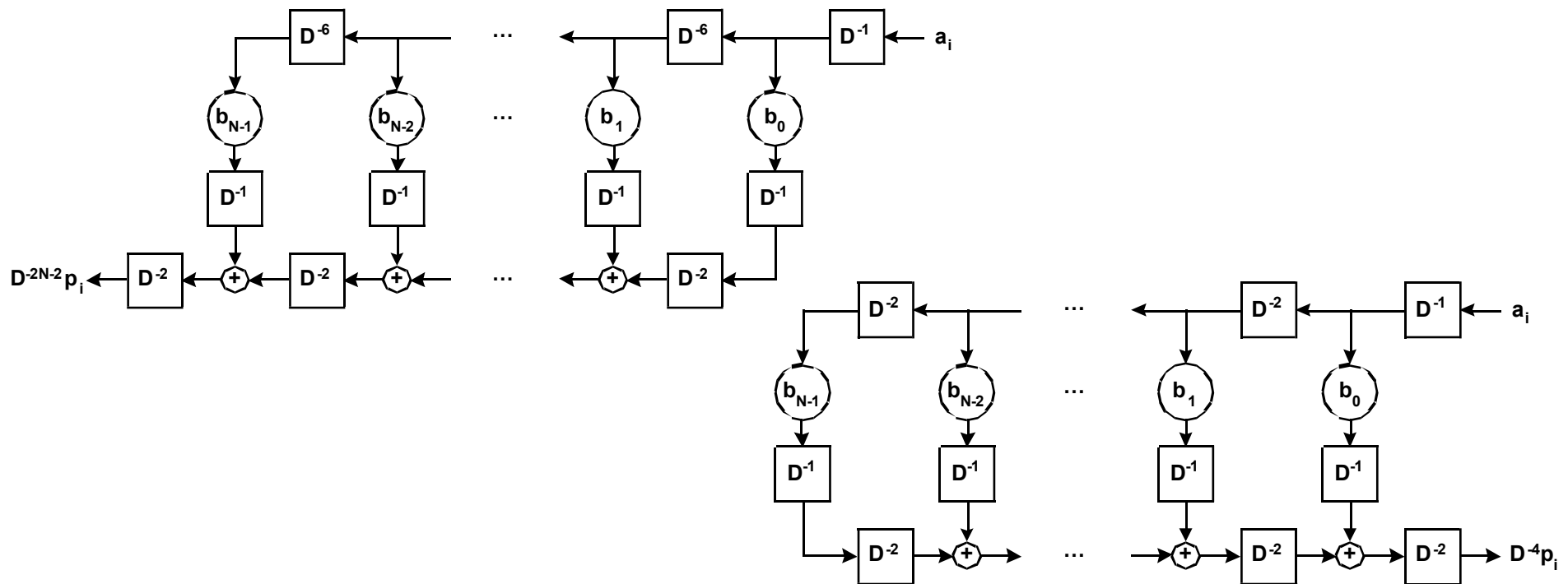
# QCA Multiplication Diagrams

- Multiplication Networks for QCA
  - One Clock Zone Delay:  $D^{-1}$  ( $D^{-4}=Z^{-1}$ )
- Filter Network Transformation Using D Operators







## Right-to-Left Networks

- Equations


$$(s_{ij}, c_{ij}) = \text{Addition} (b_j D^{-7j-2} a_i, D^{-3} s_{i(j-1)}, D^{-1} c_{i(j+1)})$$

$$= \text{Addition} (b_j a_{i-7j-2}, s_{(i-3)(j-1)}, c_{(i-1)(j+1)})$$


$$(s_{ij}, c_{ij}) = \text{Addition} (b_j D^{-6j-2} a_i, D^{-2} s_{i(j-1)}, D^{-4} c_{ij})$$

$$= \text{Addition} (b_j a_{i-6j-2}, s_{(i-2)(j-1)}, c_{(i-4)j})$$

### CSM Network

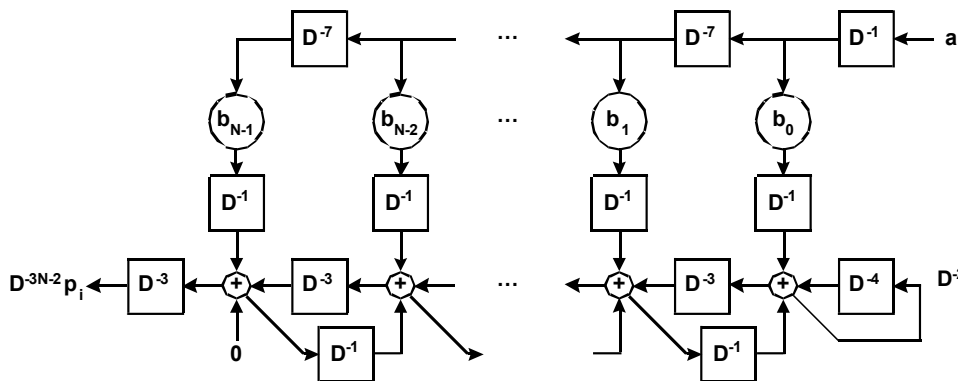

### CDM Network

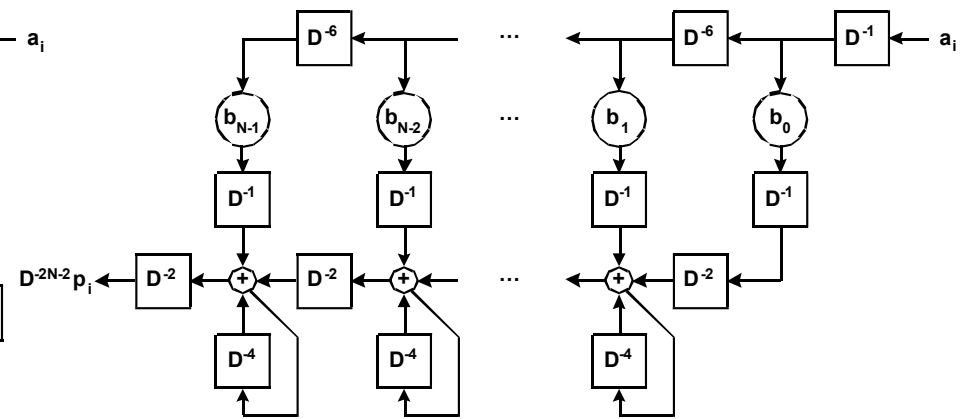



# Right-to-Right Networks

- Equations


$$(s_{ij}, c_{ij}) = \text{Addition} (b_j D^{-j-2} a_i, D^{-3} s_{i(j+1)}, D^{-1} c_{i(j-1)})$$

$$= \text{Addition} (b_j a_{i-j-2}, s_{(i-3)(j+1)}, c_{(i-1)(j-1)})$$


$$(s_{ij}, c_{ij}) = \text{Addition} (b_j D^{-2j-2} a_i, D^{-2} s_{i(j+1)}, D^{-4} c_{ij})$$

$$= \text{Addition} (b_j a_{i-2j-2}, s_{(i-2)(j+1)}, c_{(i-4)j})$$

## CSM Network

 

## CDM Network

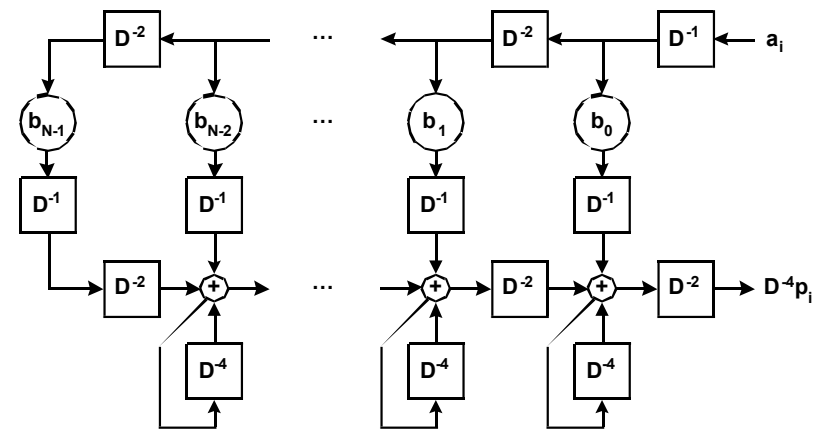




## Multiplier Block Diagrams


- Nominal Design

  - Right-to-Right CSM


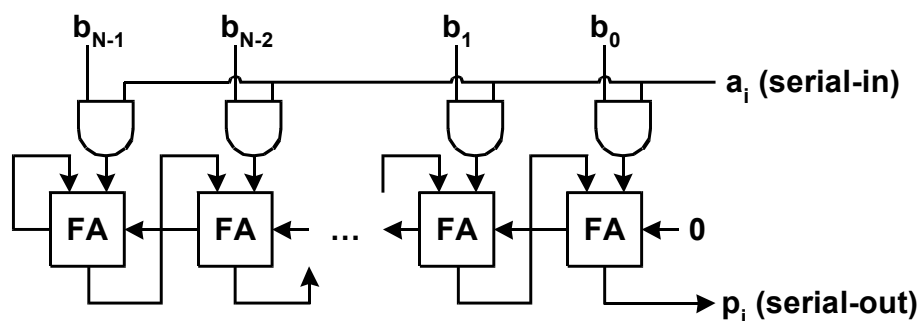




  - Right-to-Right CDM

 



## Modified Design

 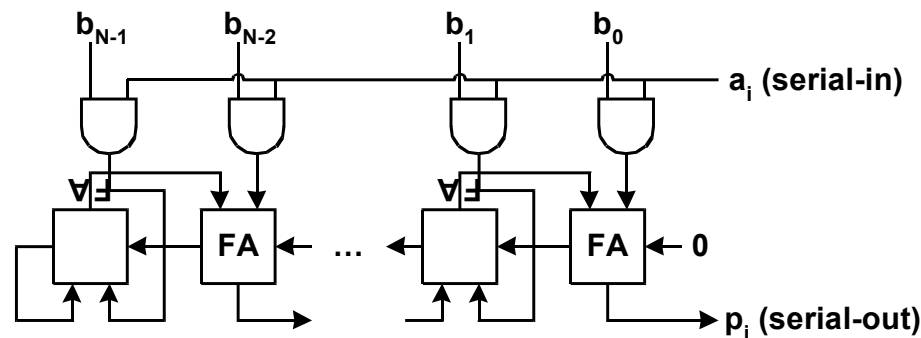



# Multiplier Design


## 4-bit and 32-bit CSM Layouts

  



# Multiplier Design

## 4-bit and 32-bit CDM Layouts

 





# Carry Shift Multipliers

Size	Complexity	Area	Latency
CSM-4	507 cells	1.04 $\mu\text{m}$ x 0.61 $\mu\text{m}$	1.25 clocks
CSM-8	1,011 cells	1.93 $\mu\text{m}$ x 0.61 $\mu\text{m}$	1.25 clocks
CSM-16	2,043 cells	3.67 $\mu\text{m}$ x 0.61 $\mu\text{m}$	1.25 clocks
CSM-32	4,299 cells	7.24 $\mu\text{m}$ x 0.67 $\mu\text{m}$	1.25 clocks
CSM-64	9,579 cells	14.3 $\mu\text{m}$ x 0.85 $\mu\text{m}$	1.25 clocks



# Carry Delay Multipliers

Size	Complexity	Area	Latency
CDM-4	406 cells	1.05 $\mu\text{m}$ x 0.47 $\mu\text{m}$	1 clock
CDM-8	903 cells	2.12 $\mu\text{m}$ x 0.47 $\mu\text{m}$	1 clock
CDM-16	1,999 cells	4.19 $\mu\text{m}$ x 0.47 $\mu\text{m}$	1 clock
CDM-32	4,575 cells	8.47 $\mu\text{m}$ x 0.65 $\mu\text{m}$	1 clock
CDM-64	11,264 cells	16.8 $\mu\text{m}$ x 0.95 $\mu\text{m}$	1 clock







# Multiplier Design
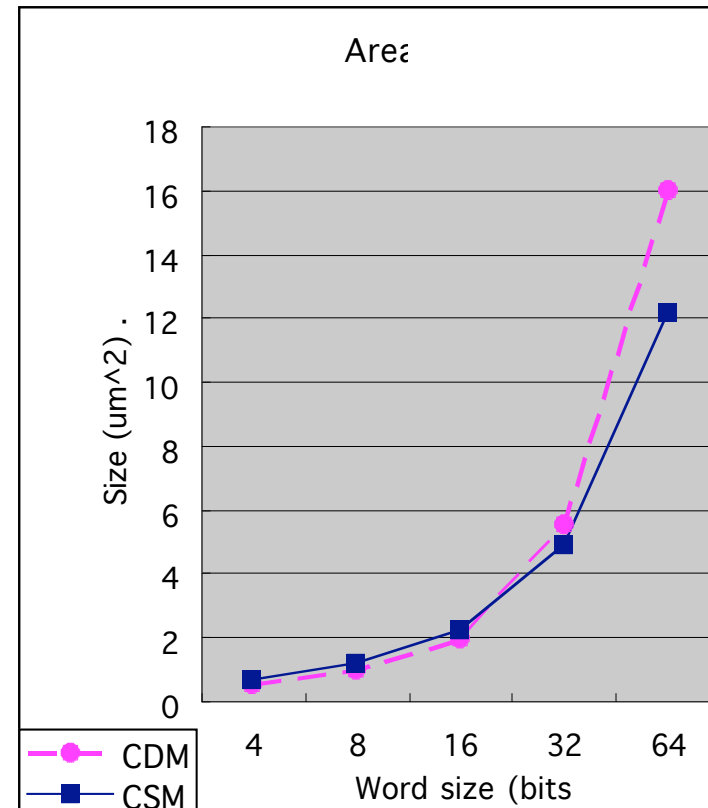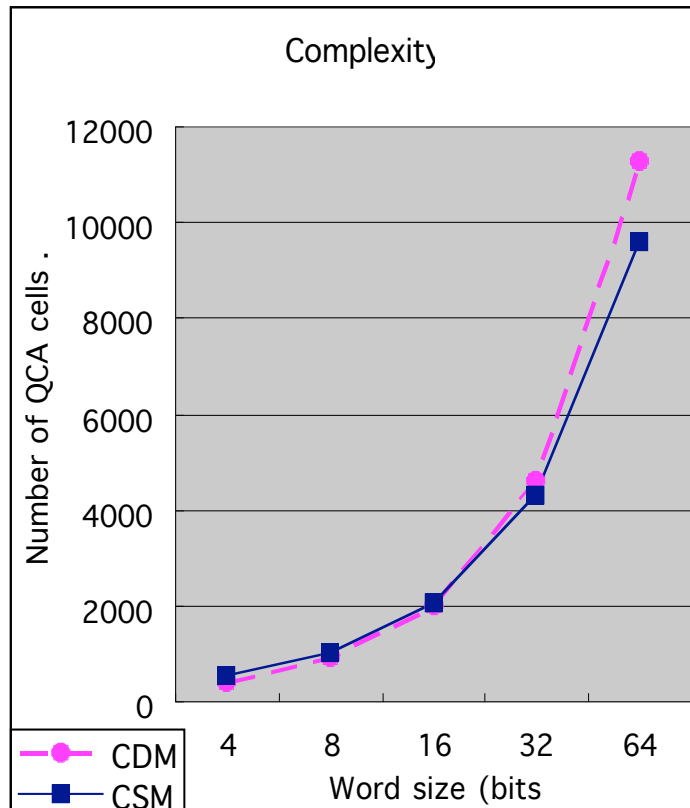
## Comparison of Different Multipliers

- Multiplier Comparisons
  - Delay: CSM=1.25 clocks, CDM=1 clock





# Conclusions

---

- Summary
  - Serial Parallel Multiplier Architecture
    - Simple Structure Chosen for Wire Delay Minimization
    - Regular Cells for Design Reuse
    - Optimized to Minimize Latency
  - Serial Parallel Multiplication Network
    - Based on Filter Network Example
    - Derived the Equations and Network Graph
  - Designed Two Serial Parallel Multipliers
    - Carry Shift Multiplier and Carry Delay Multiplier
- Contributions
  - Extended QCA Circuit Designs to Multiplication
  - Explored Various Serial Parallel Multiplication Algorithms



# QUESTIONS???